



United International University (UIU)
Dept. of Computer Science & Engineering (CSE)
MID Exam, Trimester: Fall 2024

Course Code: CSE 113/EEE 2113; Course Title: Electrical Circuits

Total Marks: 30; Duration: 1 hour 30 minutes

Any examinee found adopting unfair means would be expelled from the trimester/ program as per UIU disciplinary rules.

Question 1: Answer all the questions.

(8 Marks)

The power delivered to an element is shown in **Figure 1**. Answer the following questions: [4+4]

- i) Determine the energy absorbed by this element from 0s to 12s. CO1
- ii) Draw the energy vs time graph for the element.

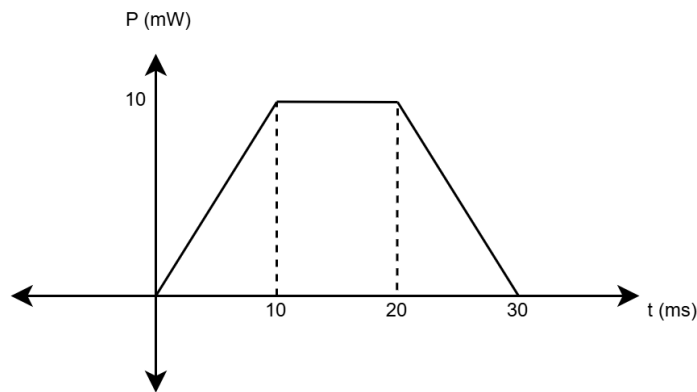


Figure 1

Question 2: Answer all the questions.

(8 Marks)

- i) Determine I and V_{ab} in the circuit shown in **Figure 2(a)** using KVL. [4+4]
- ii) Apply KCL in the circuit shown **Figure 2(a)** to determine the current through the resistors R_1 and R_3 . Furthermore, using basic Ohm's law, calculate the value of R_1 and R_3 . CO2

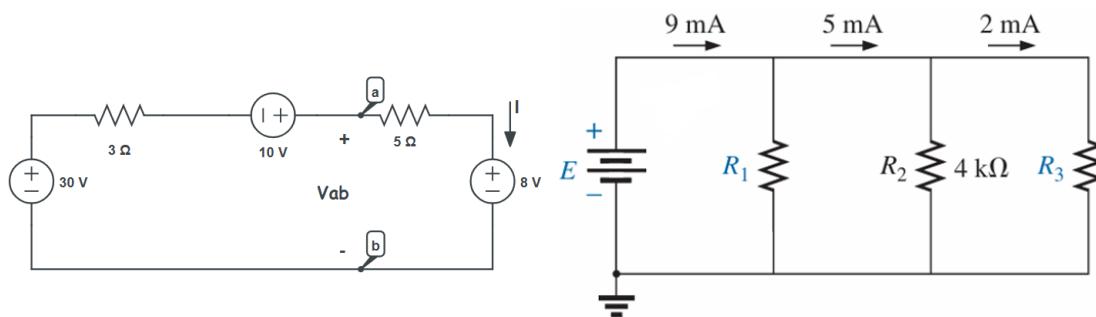


Figure 2(a)

Figure 2(b)

Question 3: Answer all the questions

(6 Marks)

Observe the circuit shown in **Figure 3** and answer the following questions:

- i) Determine the circuit's equivalent resistance. [2+1+3]
- ii) Determine the power supplied by the 5A current source. CO1
- iii) Determine the voltage of the 5Ω resistor and the current of the 4Ω resistor using VDR, CDR.

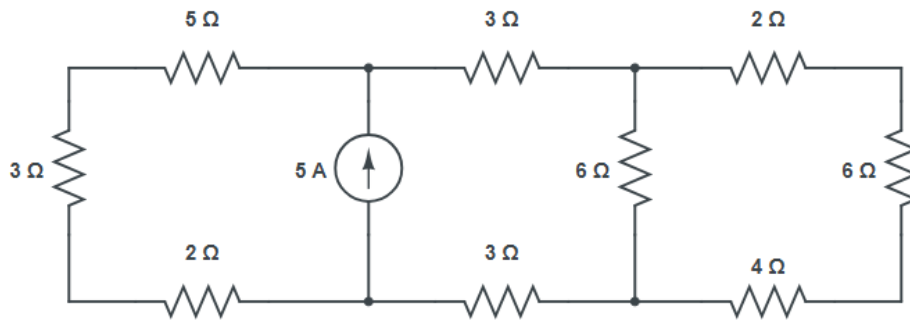


Figure 3

Question 4: Answer all the questions.

(8 Marks)

- i) Determine the voltage across 25Ω and i_0 using mesh analysis for the circuit shown in **Figure 4(a)**. [4+4]
CO2
- ii) Determine i_0 and v_0 for the circuit shown in **Figure 4(b)** using node analysis.

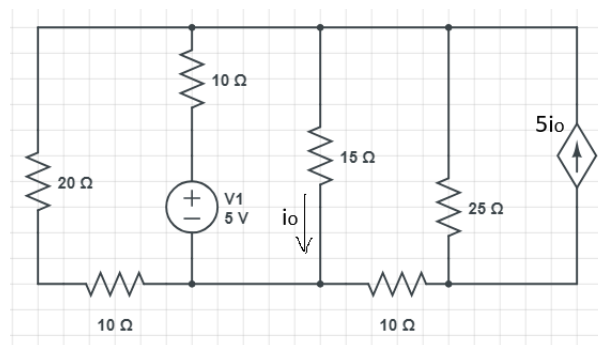


Figure 4(a)

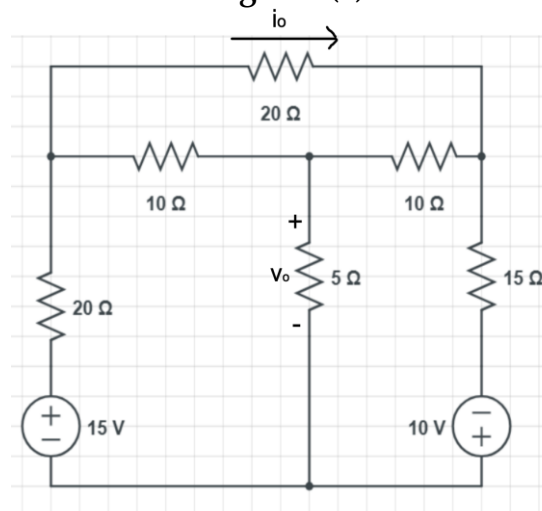


Figure 4(b)