



United International University

Dept. of Computer Science & Engineering

Trimester: Fall, 2024 (Class Test - 02)

Course No: EEE 2113

Title: Electrical Circuits


Section: L

Time: 30 minutes

Marks: 20

1. Find R_{eq} , V' , and i in the circuit below.

10

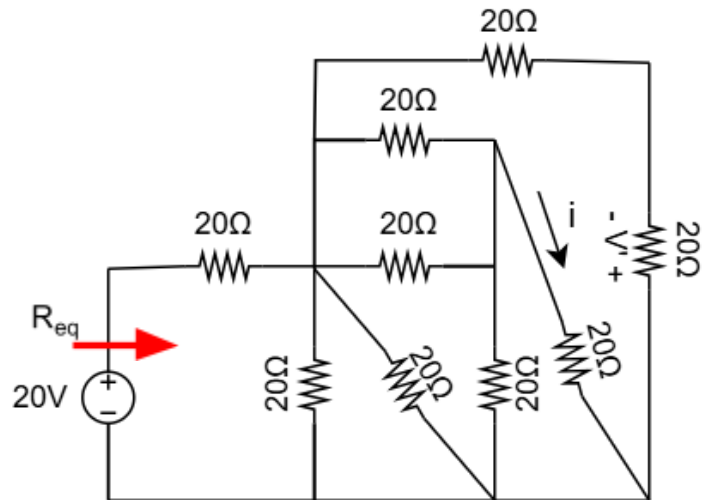

2. Using nodal analysis, find V_o and i_o in the circuit below.

10

