



# United International University

Dept. of Computer Science & Engineering

Trimester: Fall, 2024 (Class Test - 01)

Course No: EEE 2113

Title: Electrical Circuits

Section: L

Time: 30 minutes

Marks: 20

1. The energy delivered to an element is shown in figure below.


5 + 5 = 10

a) Find the power at:

I.  $t = 4 \text{ ms}$

II.  $t = 12 \text{ ms}$

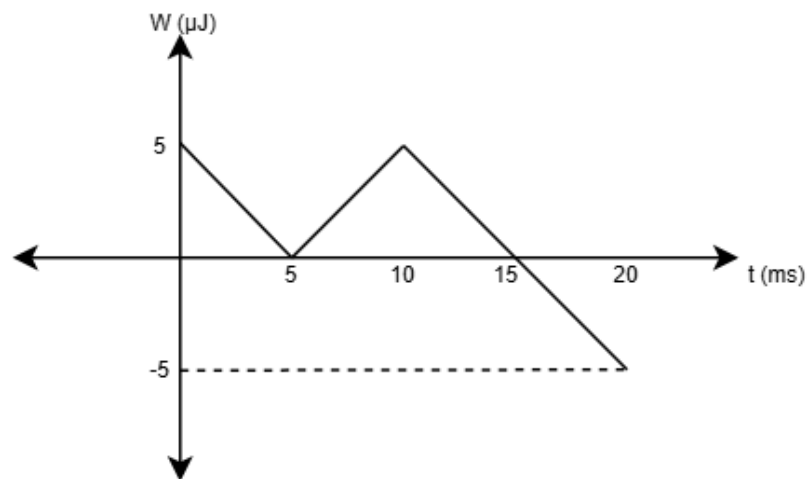b) Draw the power vs time graph for the element till  $t = 20 \text{ ms}$



2. Calculate the power supplied or absorbed by each element:

10

